

25 Spring ECEN 720: High-Speed Links: Circuits and
Systems Pre-lab Report

Lab3: Transmitter Circuits

Name: Yu-Hao Chen

UIN:435009528

Section:700

Professor: Sam Palermo

TA: Srujan Kumar Kaile

- a. Figure 8. The easiest way to do this is to run a DC sweep with $|V_{GS}|$ varying from 0 to VDD and plot the following equation.

$$f_T = \frac{g_m}{2\pi C_{gg}} \quad (1)$$

Where C_{gg} is the total gate capacitance. Comment on the results. For the f_T plot versus $|V_{GS}|$, use a linear scale for both axes. For the f_T plot versus $|I_{DS}|$, use a log scale for the x-axis (current) and a linear scale for the y-axis (frequency). Discuss how this characterization data impacts the design of high-speed circuits.



 
 


Figure 8 (a) NMOS f_T Test Circuit

(b) PMOS f_T Test Circuit

 

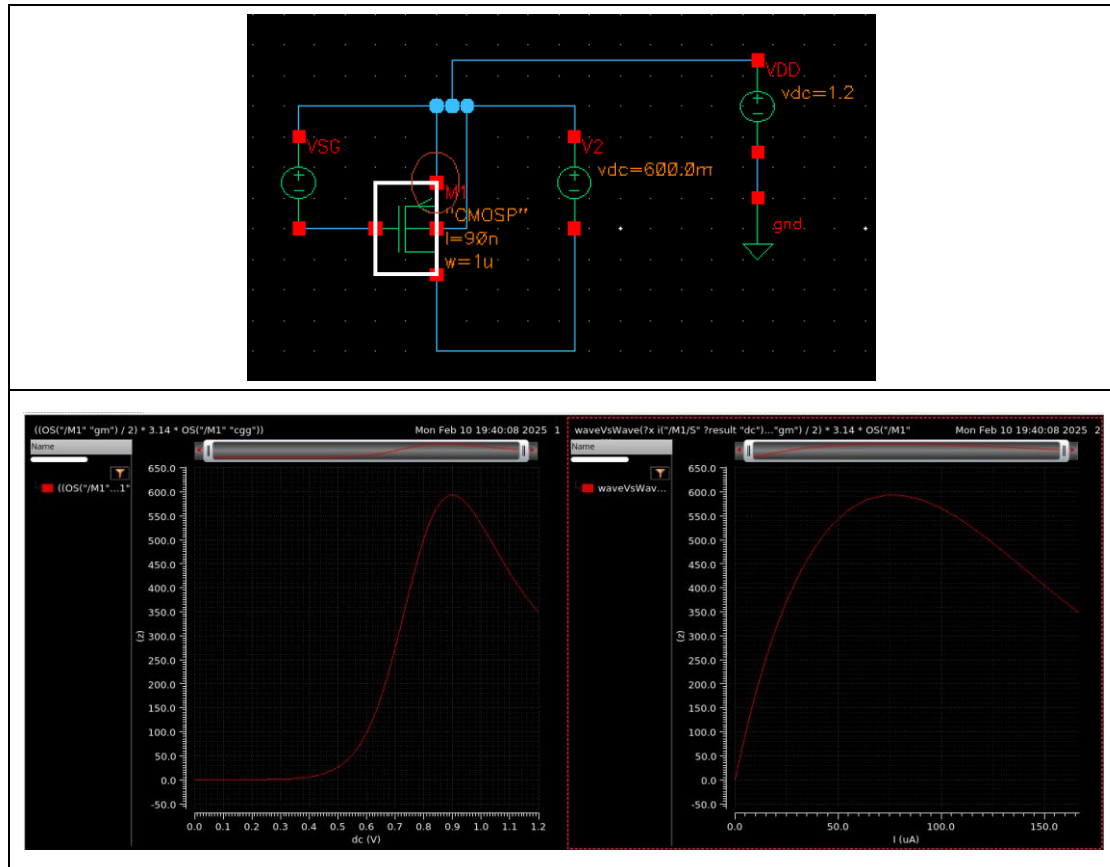

b. Find the FO4 inverter delay. The bit-rate of transmitters is often limited by the bandwidth of clock buffering. For minimum propagation delay to drive a given capacitive load, a fan-out of four inverter buffer chain (FO4 inverter delay) is often used [5]. Refer to the instructions on how to use the default 90nm CMOS technology models for more details on how to setup the test circuit. For the inverters use minimum channel length and an NMOS unit finger width of $1\mu m$. Size the PMOS/NMOS ratio of the inverter for equal rise and fall delays, measured from 50% of the input to 50% of the output. However, don't exceed a PMOS/NMOS ratio of 3, i.e., if the simulations show that a ratio greater than 3 is required for equal delay then just use 3 and accept the slight delay difference.

Sweep the supply voltage (VDD) from 0.7V to 1.2V with 50mV step size in order to include FO4 delay [ps] vs. VDD [V].

For the design of half-rate TX architecture, find optimal VDD for maximizing power efficiency at 5Gb/s data rate.


 


Figure 9 FO4 Delay Test Circuit

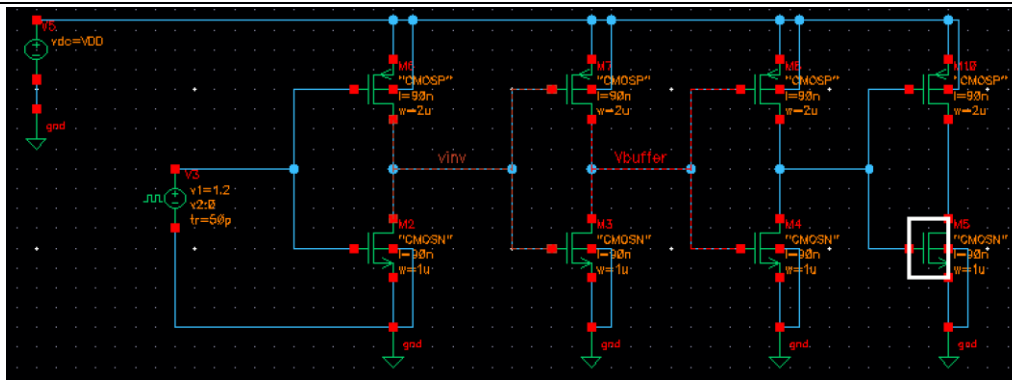

Virtuoso (R) Visualization & Analysis XL calculator@n02-hera.olympus.engr.tamu.edu

File Tools View Options Constants Help

In Context Results DB: /home/grads/h/harrison900531/cadence/simulation/pre/spectre/schematic/psf

vt vf vdc vs os op ot mp vn sp vswr hp
it if idc is opt var vn2 zp yp gd

Off Family Wave Clip Append Rectangular

Key P...
delay ?wf1 v("vinv" ?result "tran"), ?value1 VAR("VDD")/2, ?edge1 "rising", ?nth1 1, ?td1 0.0, ?tol1 nil, ?wf2 v("/vbuffer" ?result "tran"), ?value2 VAR("VDD")/2, ?edge2 "falling", ?nth2 1, ?tol2 nil, ?td2 nil, ?stop nil, ?multiple nil

Function Panel

delay

Signal1 v("/vinv" ?result "tran")
Signal2 v("/vbuffer" ?result "tran")
Threshold Value 1 VAR("VDD")/2 Threshold Value 2 VAR("VDD")/2
Edge Number 1 1 Edge Number 2 1
Edge Type 1 rising Edge Type 2 falling
Periodicity 1 1 Periodicity 2 1
Tolerance 1 nil Tolerance 2 nil
Number of occurrences single Plot/print vs. trigger

OK Apply Defaults Help Close

Function Panel Stack

status area

13 append plot to current graph

Parametric Analysis - spectre(1): lab3 pre schematic @n02-hera.olympus.engr.tamu.edu

File Analysis Help


Parametric Simulation Completed.

Run Mode: Sweeps & Ranges


Variable	Value	Sweep?	Range Type	From	To	Step Mode	Total Steps	Inclusion List	Exclusion List
VDD		✓	From/To	0.7	1.2	Auto	11		

100%

 Info: Parametric Simulation Completed
8 HelpAction



FO4 sweep

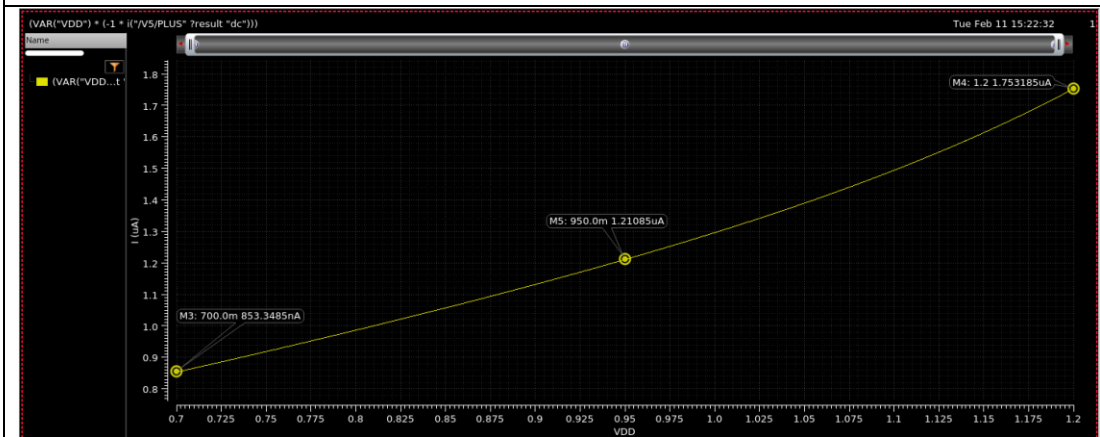

The power

	VDD	(IS("V5/..."("VDD"))	FO4
1	700.0E-3	77.62E-9	142.0E-12
2	750.0E-3	88.48E-9	102.2E-12
3	800.0E-3	100.3E-9	79.88E-12
4	850.0E-3	113.2E-9	66.86E-12
5	900.0E-3	127.4E-9	58.48E-12
6	950.0E-3	143.2E-9	53.10E-12
7	1.000	160.7E-9	49.21E-12
8	1.050	180.4E-9	46.35E-12
9	1.100	202.9E-9	44.16E-12
10	1.150	228.8E-9	42.36E-12
11	1.200	258.8E-9	41.00E-12

Finding the best operation point by power * FO4 (which is 0.9v)