

25 Spring ECEN 720: High-Speed Links: Circuits and
Systems Pre-lab Report

Lab2: Channel Models

Name: Yu-Hao Chen

UIN:435009528

Section:700

Professor: Sam Palermo

TA: Srujan Kumar Kaile

Pre-Lab

1. Plot S11 and S21 for the circuit shown in Figure 10 using Cadence (RT=50Ω).

a. Td=0ps (no t-line), C1=0pF, L1=0nH, C2=1pF

b. Td=0ps (no t-line), C1=3pF, L1=2nH, C2=1pF

c. Td=300ps , C1=3pF, L1=2nH, C2=1pF

Comment on the results.



 
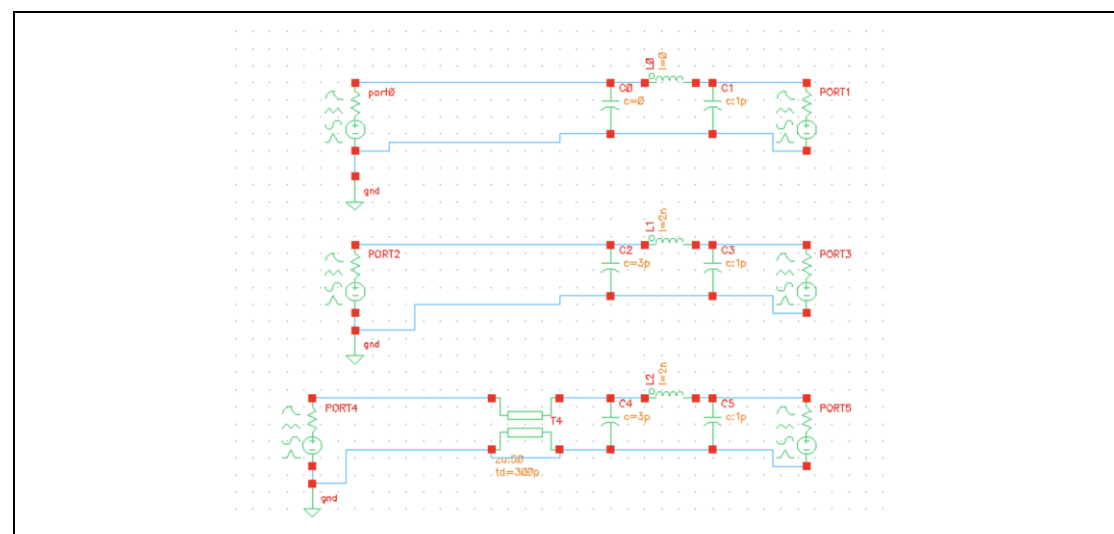


Figure 10 S-parameters Simulation Circuit

S-Parameter	Definition	Physical Meaning
S11	b_1/a_1	Input Reflection Coefficient (Return Loss at Port 1)
S22	b_2/a_2	Output Reflection Coefficient (Return Loss at Port 2)
S21	b_2/a_1	Forward Transmission (Insertion Loss, Gain, or Attenuation from Port 1 to Port 2)
S12	b_1/a_2	Reverse Transmission (Isolation or Reverse Gain from Port 2 to Port 1)

 


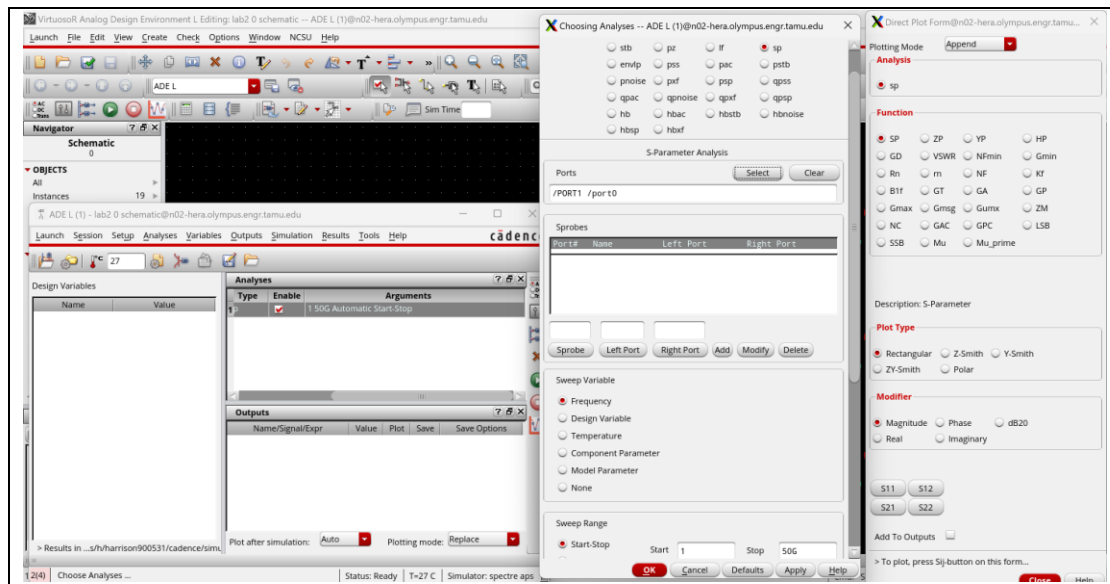

Case1


For low frequency $C = \text{open}$, no reflection $R_S = R_T$

For high frequency $C = \text{short}$, reflection $= -1$ $R_T = 0$

 

Case 2

Same condition with case1 with LC in the middle (bandpass filter will have high transmission at certain frequencies and may produce large reflections at other frequencies.)

 


Case 3

transmission line adds signal delay, but even without this wire, the LC element will still affect the impedance match, causing reflections to exist.

- In high-frequency circuits, even if there are no transmission lines, impedance matching design still needs to be considered to reduce reflections and improve signal integrity (SI).

 2. Briefly compare the difference between AC and DC coupled termination schemes.



Feature	AC Coupled Termination	DC Coupled Termination
Definition	Uses a capacitor in series to block DC components while allowing AC signals to pass.	Direct electrical connection without capacitive isolation, passing both AC and DC components.
DC Biasing	Blocks DC, requiring separate biasing networks for proper voltage levels at the receiver.	Directly maintains DC bias from the source, simplifying circuit design.
Impedance Matching	Provides impedance matching only for AC signals . Requires external biasing resistors to maintain termination impedance.	Provides continuous impedance matching for both AC and DC signals, ensuring signal integrity.
Complexity	Requires additional biasing networks, making design more	Simpler implementation since no additional biasing is needed.

	complex.	
Common Applications	High-speed digital signals (e.g., LVDS, HDMI, PCIe, RF circuits), where DC biasing differs between transmitter and receiver.	Low-frequency or DC-coupled systems (e.g., TTL, CMOS, differential signaling like USB, DDR memory), where maintaining DC level is crucial.